

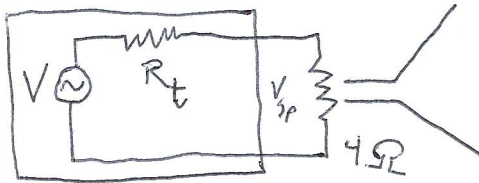
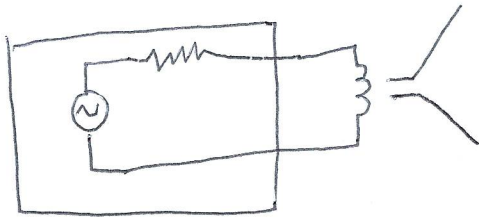


Phys 111A 29 Aug 19


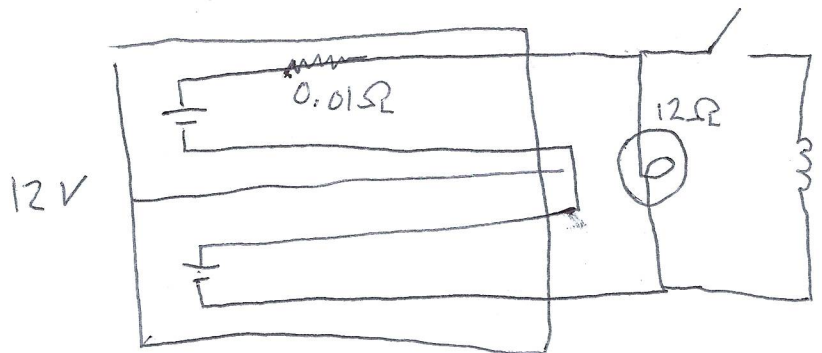


$$V_{sp} = \frac{4}{R_t + 4} V \quad R_t \rightarrow 0 \text{ for loudest speaker}$$

$R_t = \text{Output Impedance}$

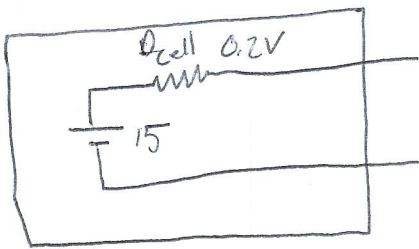


Low output impedances are good

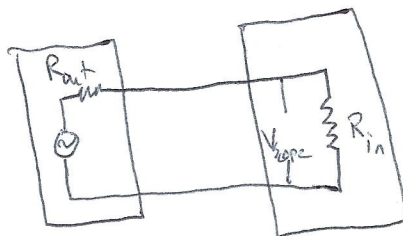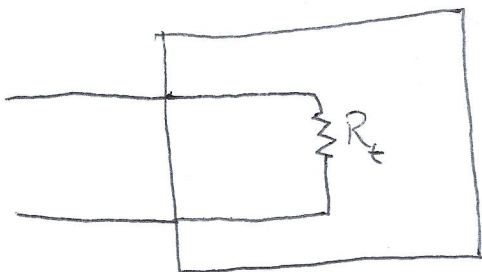

$R_t = \text{input impedance} = R_{in}$

$$V_{scope} = \frac{R_{in}}{R_{in} + R_{out}} V_s$$

Large input impedances are good

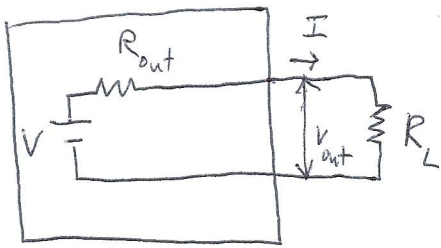

$$R_L \rightarrow \infty \quad I = 0 \quad V_{out} = V$$

$$\text{As } R_L \downarrow \quad I \uparrow \quad V_{out} \downarrow$$

$$\Delta I \quad \Delta V$$

~~$$\Delta V = V$$~~


$$\Delta V = -R_{out} \Delta I$$

$$R_{out} = -\frac{\Delta V}{\Delta I}$$

$$V_{out} = V - R_{out} I$$

$$= -\frac{\Delta V}{\Delta I}$$

### Frequency Dependent Devices

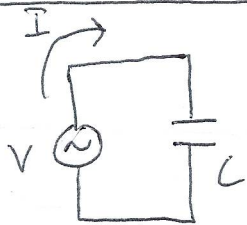

$$V = A \cos \omega t \quad Q = CV$$

$$I = \frac{dQ}{dt} = C \frac{dV}{dt}$$

$$\frac{dV}{dt} = -A \omega \sin \omega t$$

$$Z = \frac{V}{I}$$


$$\frac{A \cos \omega t}{-A \omega \sin \omega t} = \frac{1}{\omega} \cot \omega t = Z$$

$$V = e^{j\omega t}$$

$$I = j\omega e^{j\omega t}$$

$$Z = \frac{V}{I} = \frac{e^{j\omega t}}{j\omega e^{j\omega t}} = \frac{1}{j\omega}$$

Recovered Ohm's Law


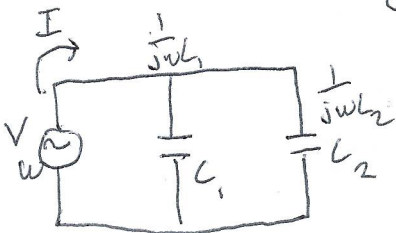


$$C_{tot} = \frac{Z_1 Z_2}{Z_1 + Z_2} = \frac{\frac{1}{j\omega C_1} \frac{1}{j\omega C_2}}{\frac{1}{j\omega C_1} + \frac{1}{j\omega C_2}} = \frac{1}{j\omega(C_1 + C_2)}$$

$$= \frac{1}{j\omega(C_1 + C_2)}$$

$$C_{tot} = C_1 + C_2$$
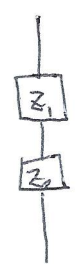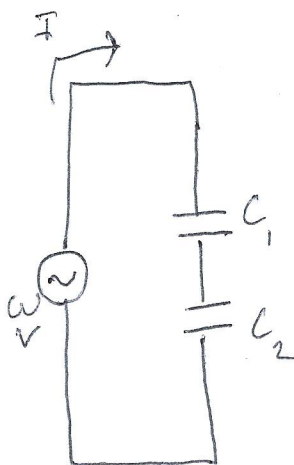
$$\frac{V}{Z_{tot}} = \frac{V}{\frac{1}{j\omega C_{tot}}} = j\omega C_{tot} V$$



$$Z_{tot} = Z_1 + Z_2 = \frac{1}{j\omega C_1} + \frac{1}{j\omega C_2}$$


$$= \frac{1}{j\omega} \left( \frac{1}{C_1} + \frac{1}{C_2} \right) = \frac{1}{j\omega} \left( \frac{C_1 + C_2}{C_1 C_2} \right)$$

$$= \frac{1}{j\omega C_{tot}}$$

$$C_{tot} = \frac{C_1 C_2}{C_1 + C_2} \quad C = \frac{\epsilon_0 A}{d}$$


$$I_{lab} = \operatorname{Re}(I)$$

$$I_m[I]$$


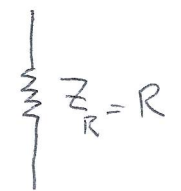


$$Z = Z_R + Z_C = R + \frac{1}{j\omega C}$$

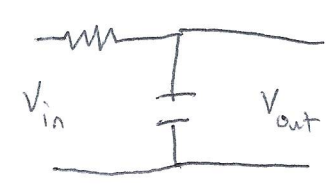$\operatorname{Re}[Z]$  = resistance  
 $\operatorname{Im}[Z]$  = reactance


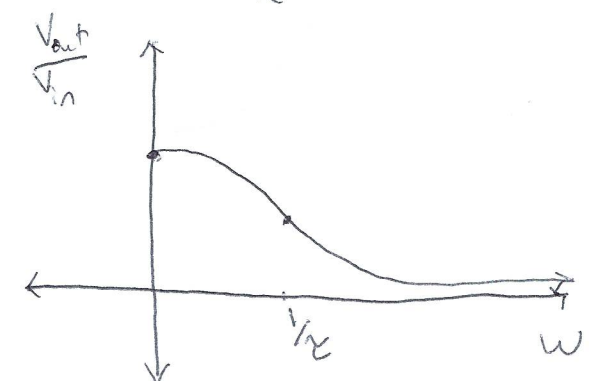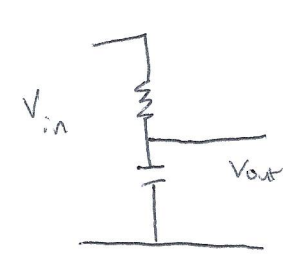
$$V_{out} = \frac{Z_C}{Z_C + Z_R} V_{in} \quad Z_R = R, \quad Z_C = \frac{1}{j\omega C}$$



$$\frac{Z_C}{Z_R} = \frac{1}{j\omega C} = \frac{1}{j\omega RC}$$

$$\frac{1}{\omega RC} = 1 \quad \omega = \frac{1}{RC}$$

$$\tau = RC$$


- a)  $\omega = 0 \quad V_{out}/V_{in} = \infty$
- b)  $\omega = \infty \quad V_{out}/V_{in} \Rightarrow 0$
- c) construct dimensionless parameter
- d) breakpoint

$$\frac{V_{out}}{V_{in}} = \frac{1}{j\omega C} = \frac{1}{j\omega RC + 1} = \frac{1}{1 + j\omega \tau}$$

$$\omega_0 = \frac{1}{\tau}$$

$$\frac{V_{out}}{V_{in}} = \frac{1}{1 + j\omega \omega_0 \tau}$$

$$\left| \frac{V_{out}}{V_{in}} \right| = \left( \frac{1}{1 + \left(\frac{\omega}{\omega_0}\right)^2} \right)^{1/2}$$

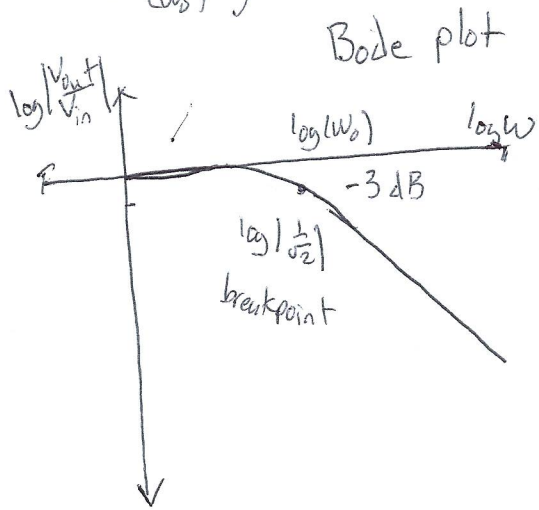

$$T = 20 \log_{10} \left| \frac{V_{out}}{V_{in}} \right|$$


decibels

$$\frac{V_{out}}{V_{in}} = \frac{1}{10} = -20 \text{ dB}$$

$$P \propto V^2$$




$$P \propto \frac{1}{100} \text{ for } -20 \text{ dB}$$
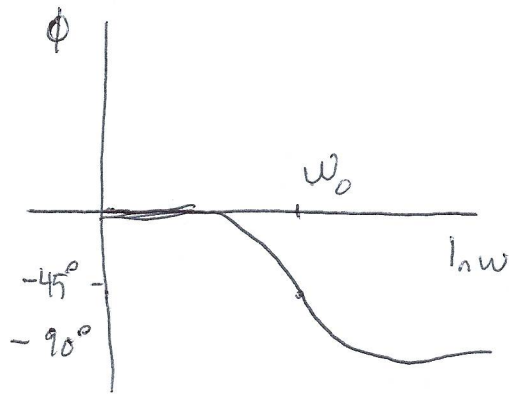
$$\phi = \tan^{-1} \frac{\text{Im}(V_{out})}{\text{Re}(V_{out})}$$




Phys 111A 19 Sept 19

## Bipolar Transistor

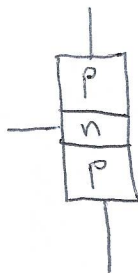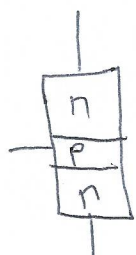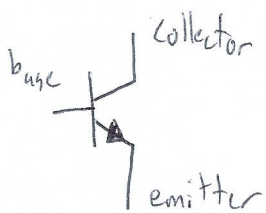

## Mosfet / MOSFET

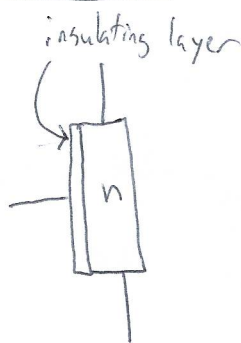



Old ones  
Burn out easily

Junction






JFET

Field Effect Transistor


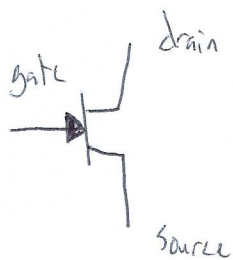


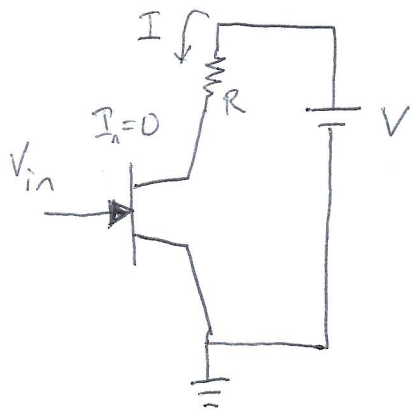

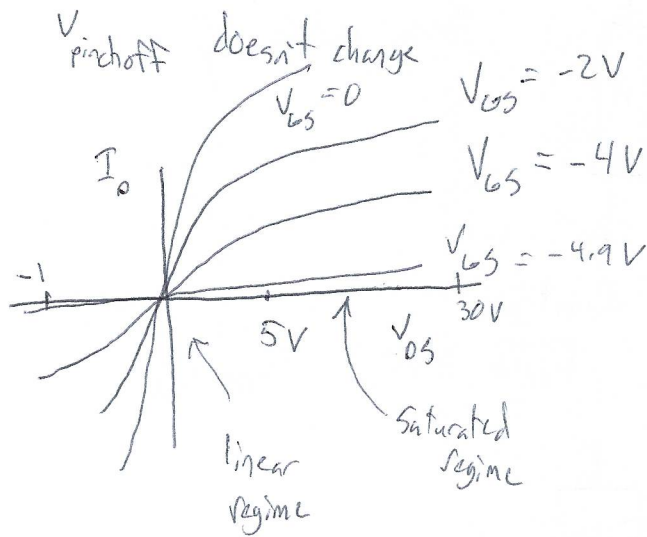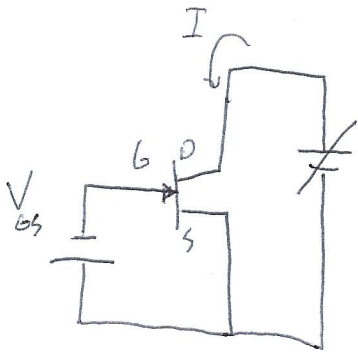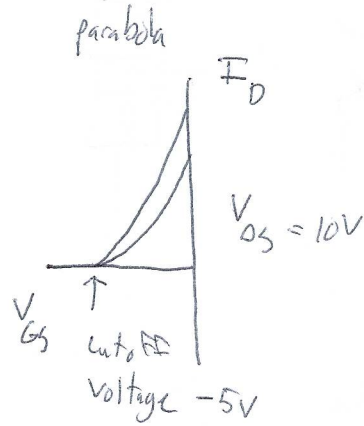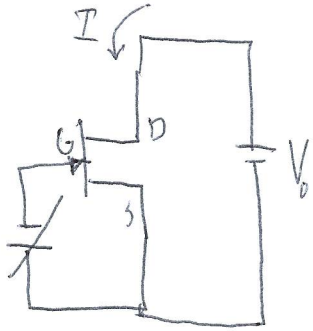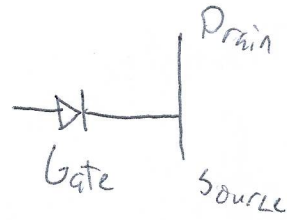Burn it out by flowing current through gate





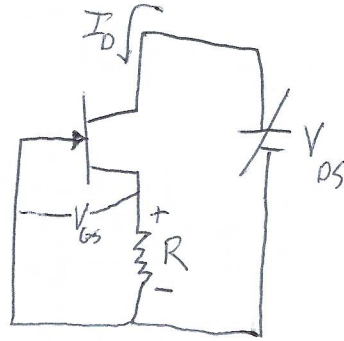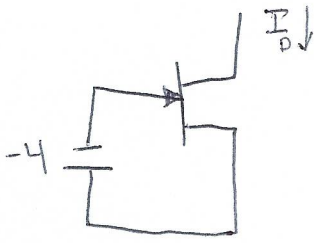Goal:  $\Delta I_D = 0$  for any  $V_{DS} > 5V$




~~$I_D = 0$   $V_{GS} = 0$  not possible condition~~

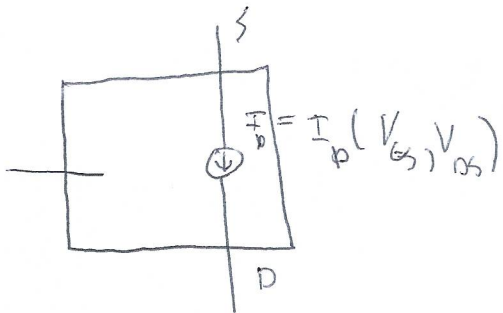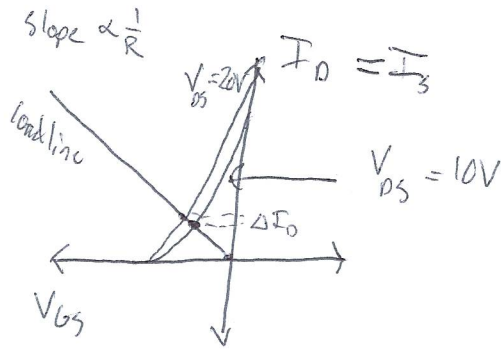~~$I_D = \text{large}$   $V_{GS} = -\text{large}$  not possible condition~~




$$V_{GS} = V_{GS_0} + V_{GS}$$

$$I_D = I_{D_0} + I_d$$

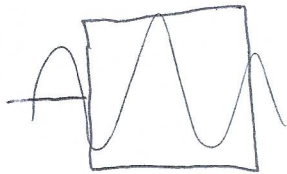


$g_m = \text{transconductance}$

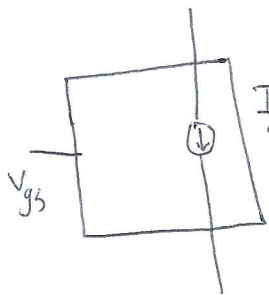



$$I_d = g_m V_{GS}$$

$$g_m = \left. \frac{\partial I_D}{\partial V_{GS}} \right|_{V_{DS}}$$

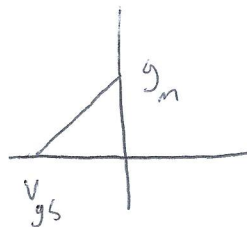

# Follower Circuit

Taylor series model

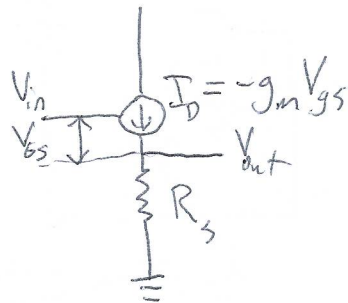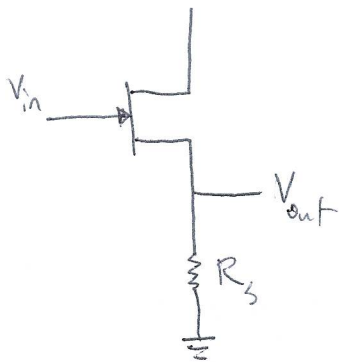

$$V_{out} = I_D R_s = -g_m V_{gs} R_s$$

$$V_{gs} = V_{in} - V_{out}$$

$$V_{out} = -g_m R_s (V_{in} - V_{out})$$

$$V_{out} (1 + g_m R_s) = -g_m R_s V_{in}$$

$$V_{out} = \frac{+g_m R_s}{1 + g_m R_s} V_{in} = \frac{+1}{1 + \frac{1}{g_m R_s}} V_{in} \quad g_m R_s \gg 1$$

$$V_{out} \approx V_{in}$$


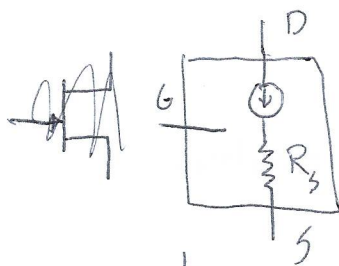



figure of  
imagination

$$r_s = \frac{1}{g_m}$$

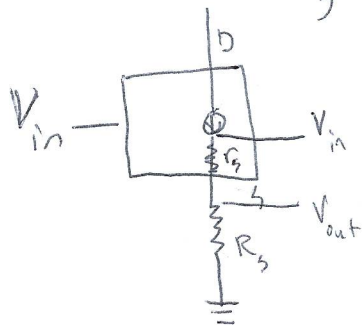
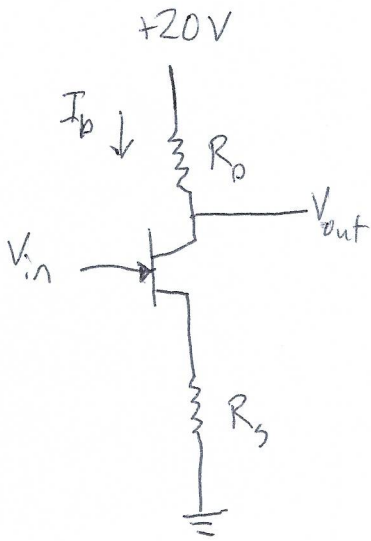
$$V_{out} = \frac{R_s}{r_s + R_s} V_{in} = \frac{1}{1 + \frac{r_s}{R_s}} V_{in} = \frac{1}{1 + \frac{1}{g_m R_s}} V_{in}$$





$$I_D =$$

$$I_D = \frac{V_{out} + 20V}{R_D} \Rightarrow \frac{V_{out} + 20V}{R_D}$$

$$= \left( \frac{V_{in}}{1 + R_S/R_S} \right) \frac{1}{R_S} = \frac{V_{in}}{R_S}$$

$$V_{out} = \cancel{20V} - R_D I_D$$


$$V_{out} = -\frac{R_D}{R_S} V_{in}$$



Phys IIIA 24 Sep 19

intrinsic

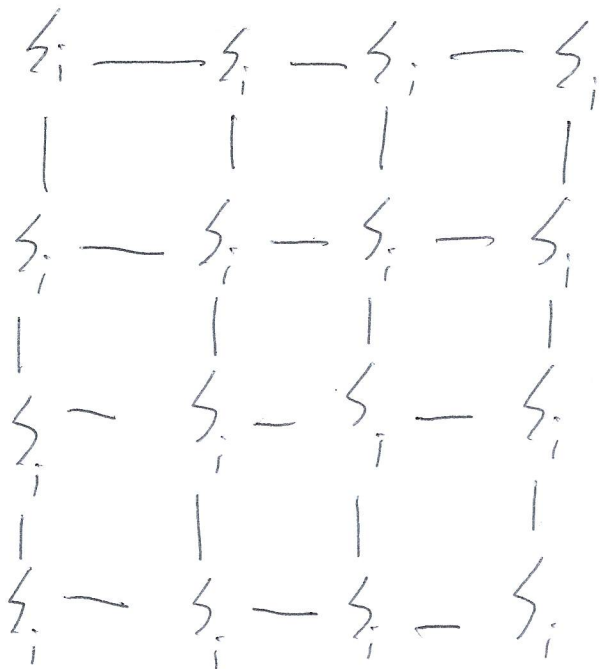
$$np = 10^{20} \frac{1}{\text{cm}^2} @ 300\text{K}$$



Thermal excitations  
cause bond breakage  
and loose electron is born  
This creates moving hole

Carriers electrons  $n = 10^{10} \frac{1}{\text{cm}^3}$   
hole  $p = 10^{10} \frac{1}{\text{cm}^3}$


n-type

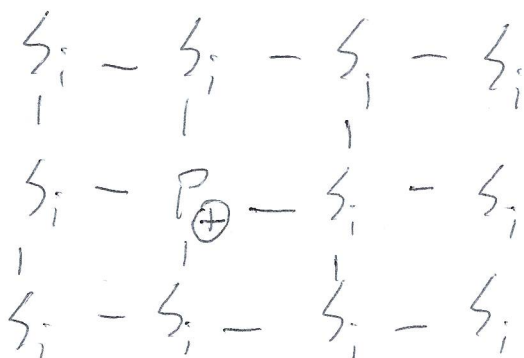

$$n = 10^{15}$$


$$p = 10^5$$

p-type

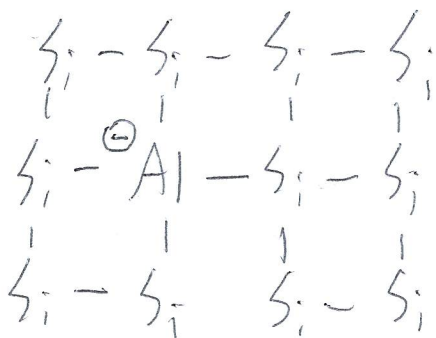


$$n = 10^5$$



$$p = 10^{15}$$

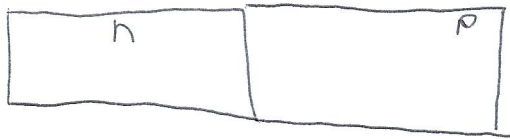



Diffusion

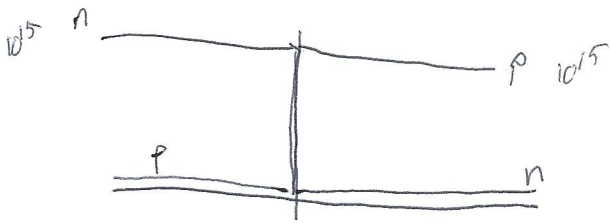





$$\Gamma = -D\nabla n + \mu E$$

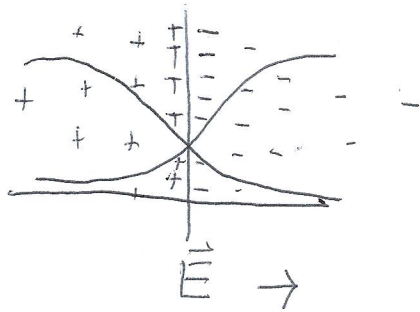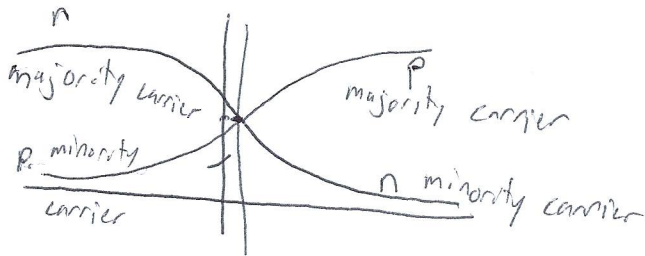

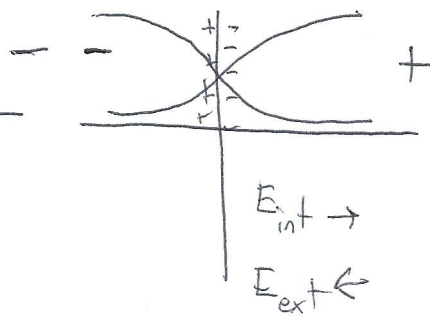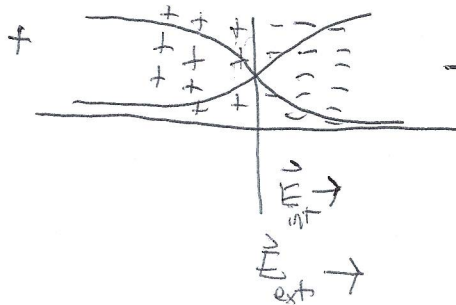acts against Diffusion  
which sets up equilibrium






# JFET

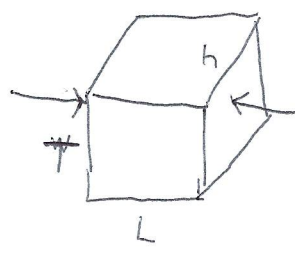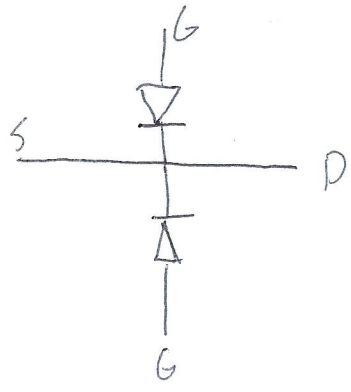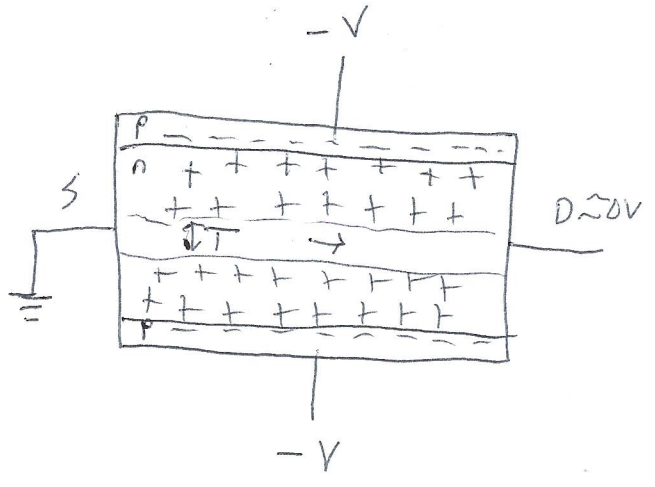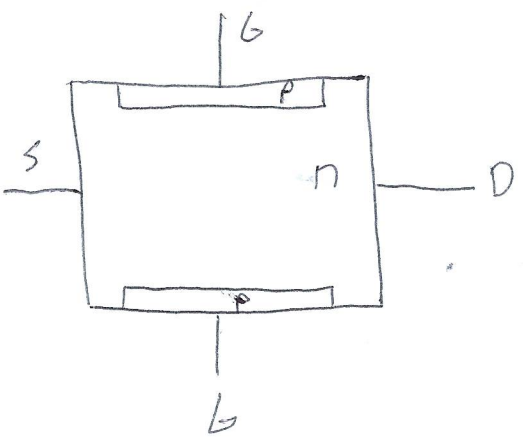


$$R = \rho \frac{L}{A}$$

$$R = \rho \frac{L}{hT}$$

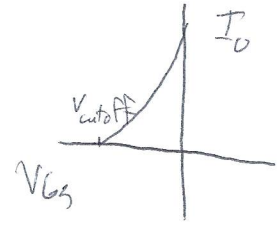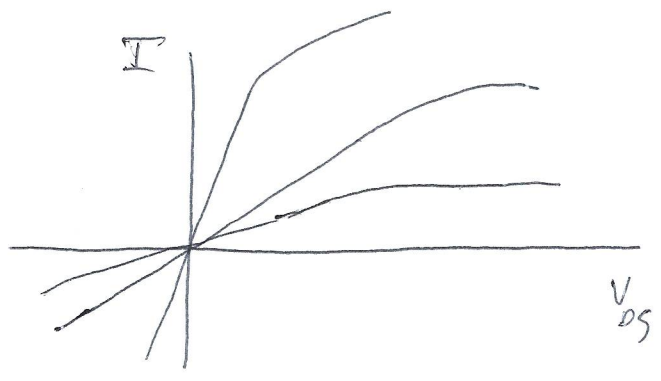

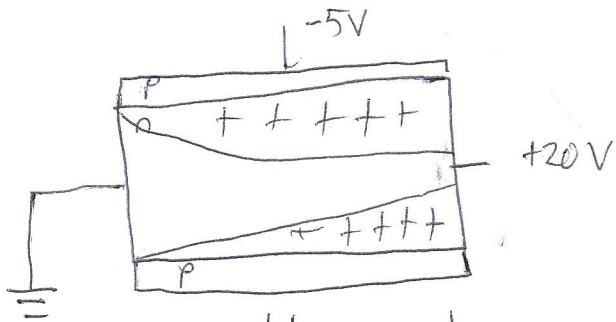


Not correct

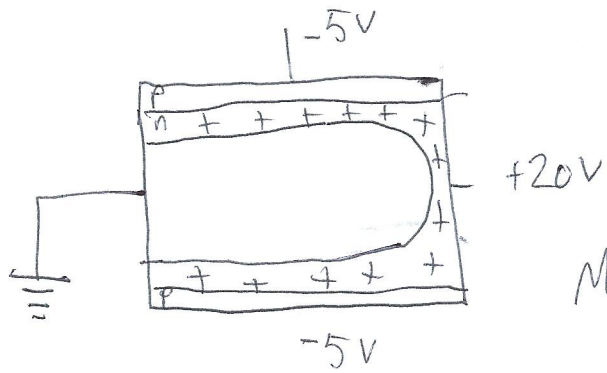

Mos + resistance is at the end!

Phys 111A 03 Oct 19

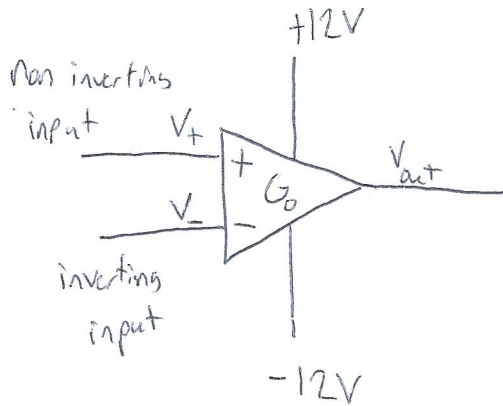

$$V_{out} = G_0 (V_+ - V_-)$$

$$G_0 = 10^5 - 10^7$$

it is huge!

Positive Feedback  
reinforcing Feedback  
"sucks" "useless"  
"unstable"


Negative Feedback

### Golden Rules


A) Inputs draw no current

B) Op-Amp will do whatever it takes to make  $V_+ = V_-$

### Follower

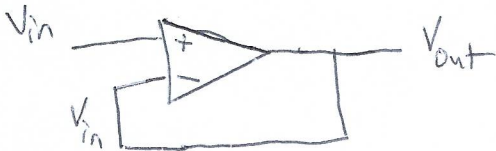

## Inverting Amplifier

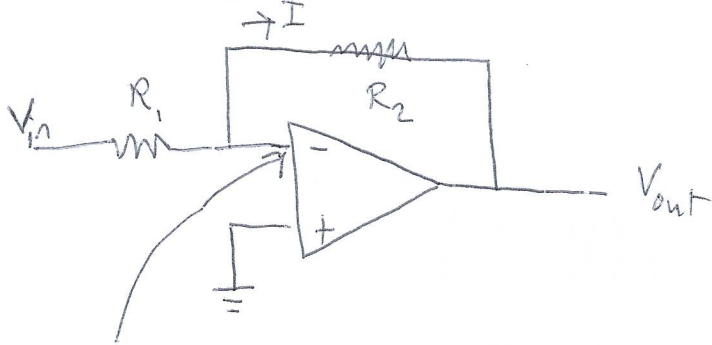


Virtual ground

$$I = \frac{V_{in}}{R_1} = -\frac{V_{out}}{R_2}$$

$$V_{out} = -\frac{R_2}{R_1} V_{in}$$

$$G = -\frac{R_2}{R_1}$$

## Noninverting amplifier

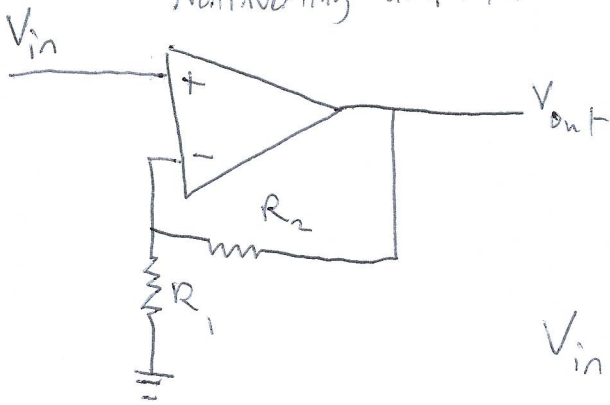


$$V_{out} = G V_{in}$$

$$V_{in} = V_- = \frac{R_1}{R_1 + R_2} V_{out}$$

$$V_{out} = \frac{R_1 + R_2}{R_1} V_{in} = \left(1 + \frac{R_2}{R_1}\right) V_{in}$$

$$G = 1 + \frac{R_2}{R_1}$$



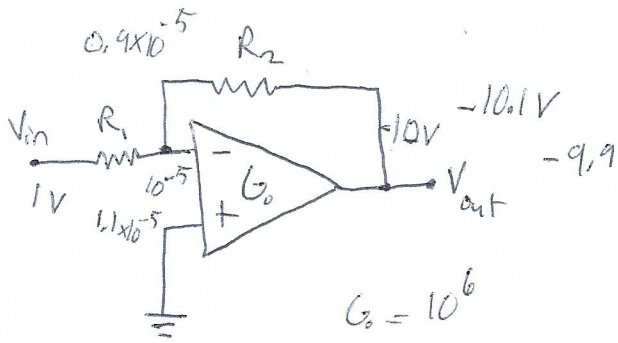

$$V_{out} = -G_0 V_-$$

$$V_- = V_{in} + \frac{R_1}{R_1 + R_2} (V_{out} - V_{in})$$


$$\frac{-V_{out}}{G_0} = V_{in} + \frac{R_1}{R_1 + R_2} (V_{out} - V_{in})$$

$$-R_1 V_{out} - \frac{V_{out}(R_1 + R_2)}{G_0} = (R_1 + R_2)V_{in} - R_1 V_{in}$$


$$-R_1 V_{out} \left(1 + \frac{R_1 + R_2}{R_1 G_0}\right) = R_2 V_{in}$$

$$V_{out} = -\frac{R_2}{R_1} \left( \frac{1}{1 + \frac{R_2 + R_1}{G_0}} \right) V_{in} \quad \frac{1 + \frac{R_2}{R_1}}{G_0}$$
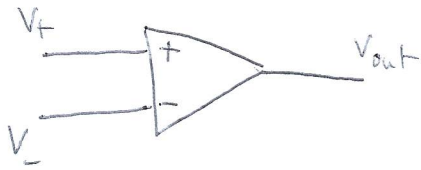
$$G = \frac{R_2}{R_1} \quad V_{out} = -\frac{G V_{in}}{1 + \frac{1+G}{G_0}} = -G V_{in}$$



$$V_{out} = -G_o (V_+ - V_-)$$

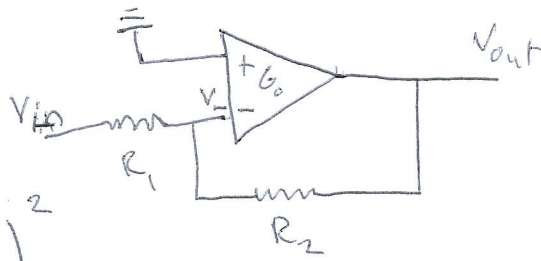

$$V_{out} = -G_o (V_-)$$

$$V_- = \pm \sqrt{\frac{-V_{out}}{G_o}}$$

$$V_- = V_{in} + \frac{R_1}{R_1 + R_2} (V_{out} - V_{in})$$

$$\pm \sqrt{\frac{-V_{out}}{G_o}} = V_{in} + \frac{R_1}{R_1 + R_2} (V_{out} - V_{in})$$

$$\pm \frac{R_1 + R_2}{R_1} \sqrt{\frac{-V_{out}}{G_o}} = \frac{R_1 + R_2}{R_1} V_{in} + V_{out} - V_{in} = \frac{R_2}{R_1} V_{in} + V_{out}$$

$$-V_{out} = \frac{R_2}{R_1} V_{in} \mp \left(1 + \frac{R_2}{R_1}\right) \sqrt{\frac{-V_{out}}{G_o}} \quad G = \frac{R_2}{R_1}$$

$$V_{out} = -G V_{in} \pm (1 + G) \sqrt{\frac{-V_{out}}{G_o}}$$

$$= -G V_{in} \left(1 \mp \frac{(1 + G)}{G V_{in}} \sqrt{\frac{-V_{out}}{G_o}}\right) = -G V_{in} \left(1 \mp \left(1 + \frac{1}{G}\right) \sqrt{\frac{-V_{out}}{G_o V_{in}^2}}\right)$$


Assume  $V_{out} = -G V_{in}$

$$V_{out} = -G V_{in} \left(1 \mp \left(1 + \frac{1}{G}\right) \sqrt{\frac{G V_{in}}{G_o V_{in}^2}}\right) \quad G_o \gg G/V_{in}$$

$$V_{out} = -G V_{in} (1 + 0) = -G V_{in}$$

# Golden Rules

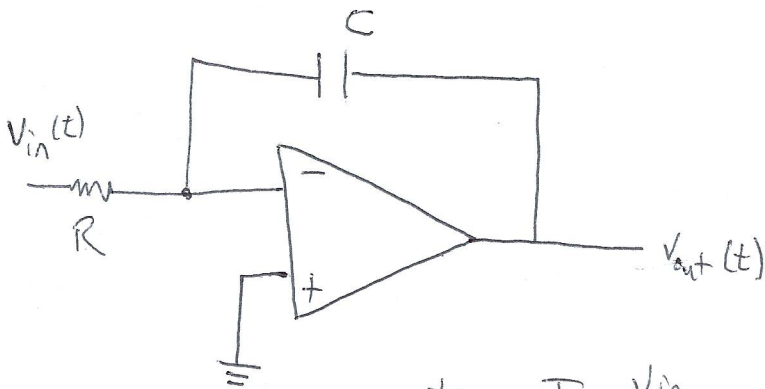- 1) Inputs draw no current
- 2) OpAmp will do whatever it takes to make  $V_+ = V_-$





$$I = \frac{V_{in}}{R} = -C \frac{dV_{out}}{dt}$$

$$\frac{dV_{out}}{dt} = -\frac{V_{in}}{\tau} \quad \tau = RC$$

$$V_{out} = -\frac{1}{\tau} \int_{-\infty}^t dt V_{in}(t)$$

or  
0

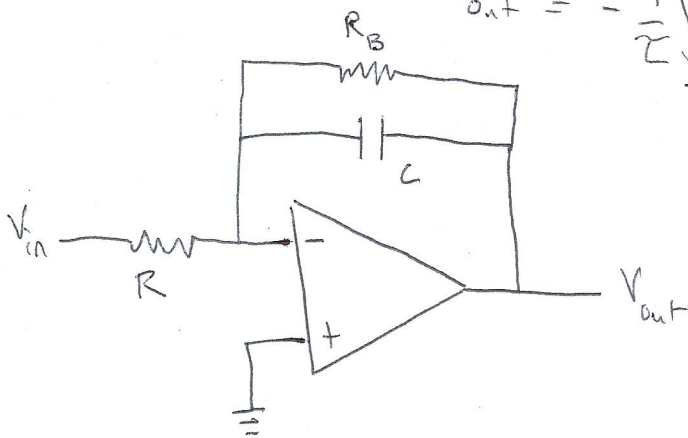

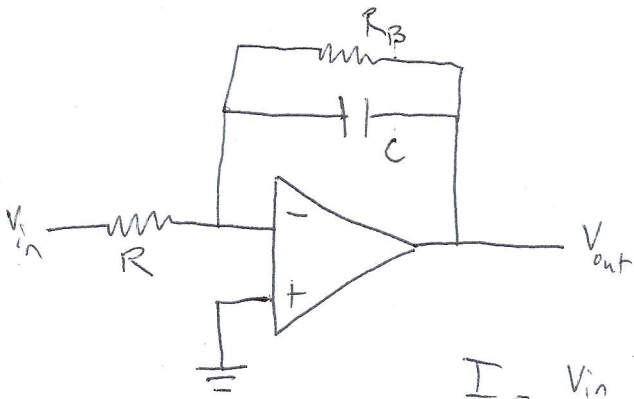

$$I = \frac{V_{in}}{R} = -C \frac{dV_{out}}{dt} - \frac{V_{out}}{R_B}$$

$$\frac{dV_{out}}{dt} + \frac{V_{out}}{\tau_B} = -\frac{V_{in}(t)}{\tau}$$

$$\tau_B = R_B C$$

$$\frac{dV_{out}}{dt} + \frac{V_{out}}{\tau_B} = 0 \Rightarrow e^{-t/\tau_B} = V_{out}$$


$$V_{out}(t) = f(t) e^{-t/\tau_B}$$

$$+ \frac{1}{\tau_B} e^{-t/\tau_B} f(t) - \frac{1}{\tau_B} e^{-t/\tau_B} f(t) + e^{-t/\tau_B} \frac{df}{dt} = \frac{dV_{out}}{dt}$$

$$\frac{df}{dt} = e^{t/\tau} V_{in}(t) \quad f(t) = \frac{1}{\tau} \int_{-\infty}^t d\tilde{t} e^{+\tilde{t}/\tau_B} V_{in}(\tilde{t})$$

$$V_{out} = \frac{e^{-t/\tau_B}}{\tau} \int_{-\infty}^t d\tilde{t} e^{\tilde{t}/\tau_B} V_{in}(\tilde{t}) = \frac{1}{\tau} \int_{-\infty}^t d\tilde{t} e^{-(t-\tilde{t})/\tau_B} V_{in}(\tilde{t})$$

Convolution integral

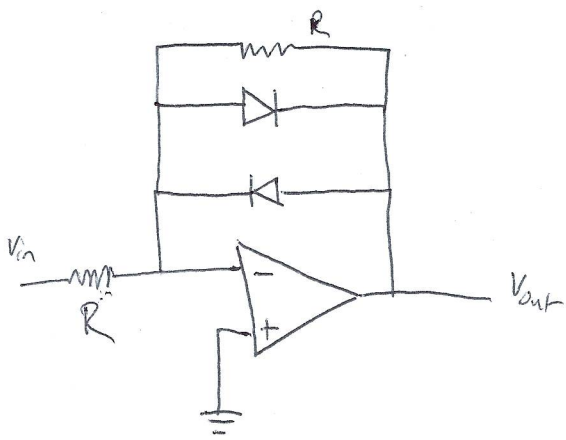




$$V_{out} =$$

$$I = \frac{V}{R}$$

$$V_{out} =$$


clips signal

input

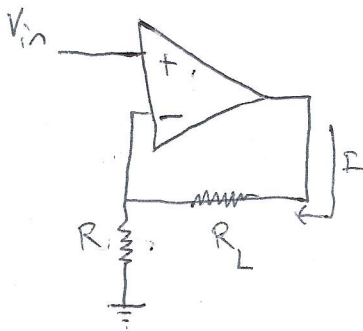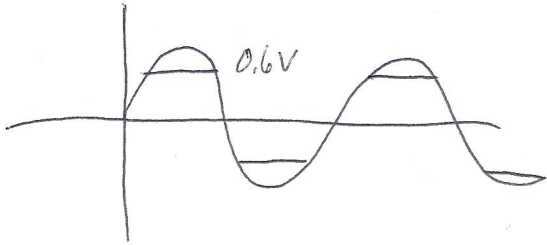
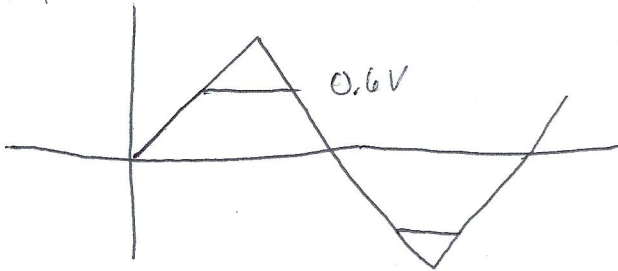


~~$$I = \frac{V_{in}}{R}$$~~

$$I = \frac{V_{in}}{R}$$

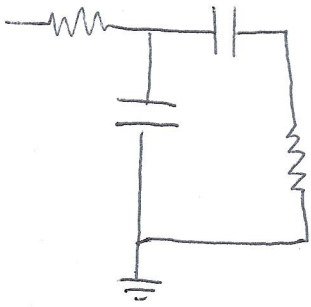

Bandpass filters

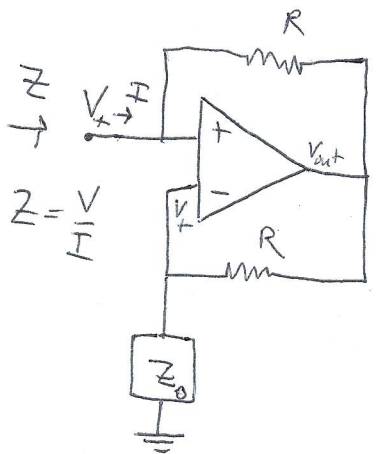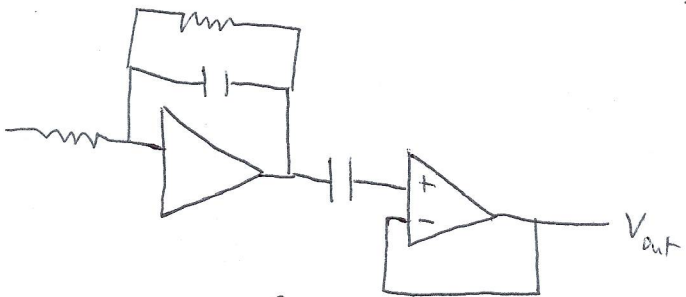

$$V_+ = V_- = \frac{Z V_{out}}{R + Z} \Rightarrow V_{out} = \frac{R + Z_0}{Z_0} V_+ = \left(\frac{R}{Z_0} + 1\right) V_+$$

$$I = \frac{V_+ - V_{out}}{R} = \frac{V_+ - \left(\frac{R}{Z_0} + 1\right) V_+}{R} = -\frac{V_+}{Z_0}$$

$$Z = -Z_0$$





NIC  
Negative Impedance  
Converter

2 NICs → gyrator


$$Z_0 = \frac{1}{j\omega C} \text{ capacitor}$$

$$Z = j\omega C R^2 \text{ inductor}$$

Phys IIIA 15 Oct 19

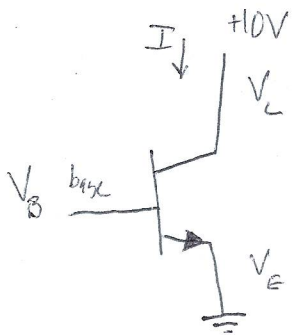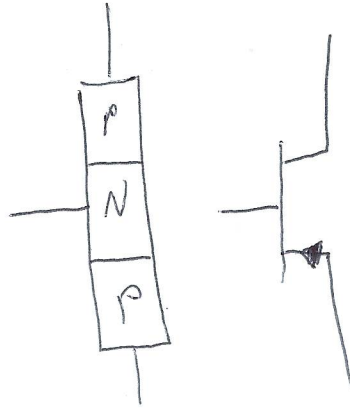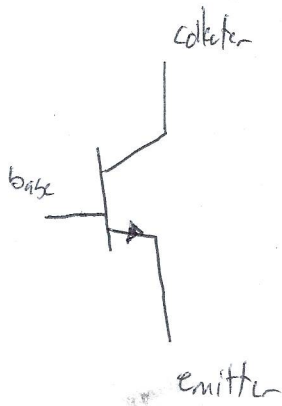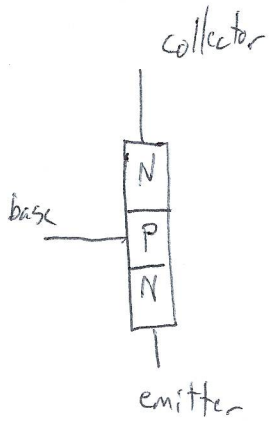


$V_B > 0.65V$  current flows

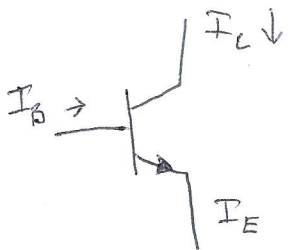

$$I_C + I_B = I_E$$


$$I_C = \beta I_B = h_{FE} I_B$$

Darlington Configuration


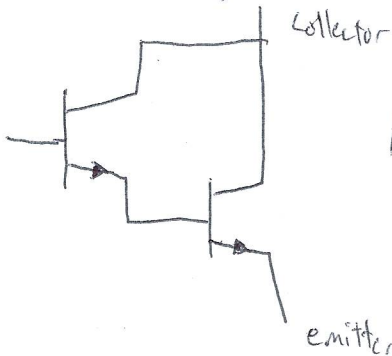


$$\beta = \beta_1 \beta_2$$

follower

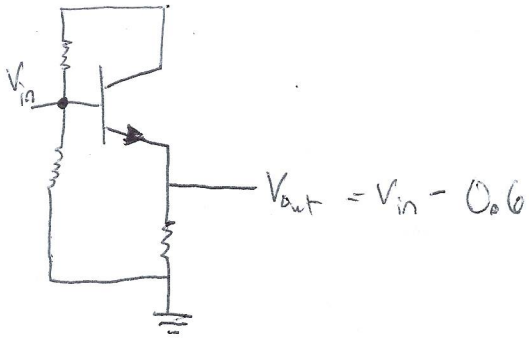


Push-pull circuit

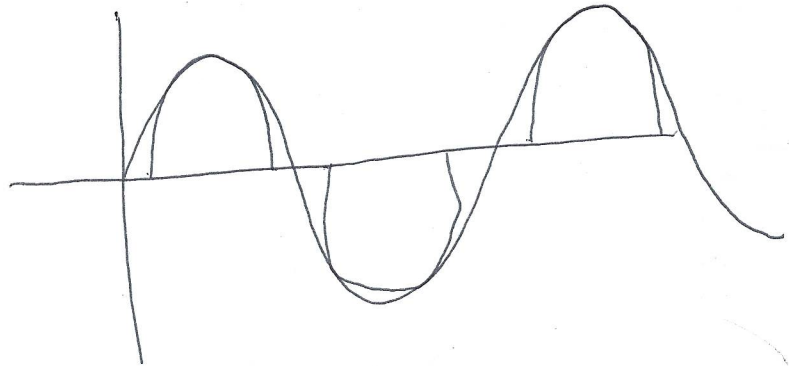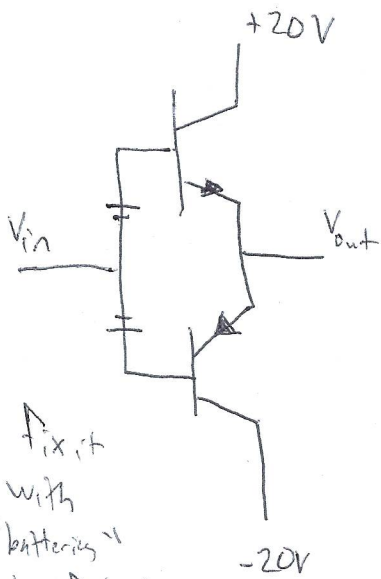

fix it  
with  
"batteries"  
to fill the  
0.6V hole

Noise

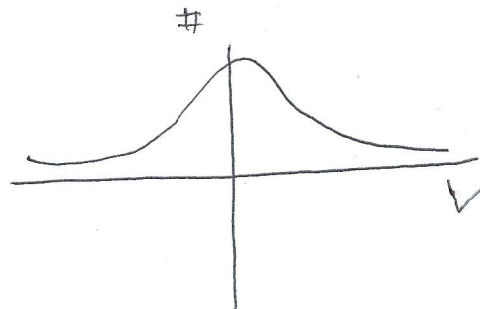



Two independent processes

$$A \rightarrow X \quad B \rightarrow Y$$






$$P_A(x) \quad P_B(y)$$










$$Z = X + Y$$




$$P_A(x=0) \times P_B(y=Z) \quad P_A(x=\frac{Z}{2}) \times P_B(y=\frac{Z}{2})$$

$$P_A(x=Z) \times P_B(y=0)$$

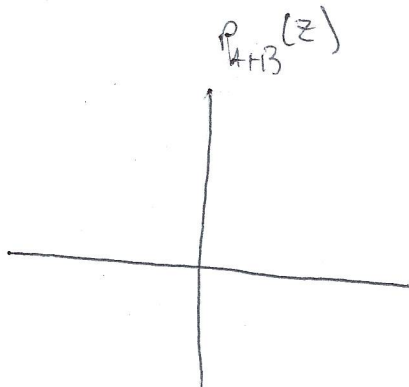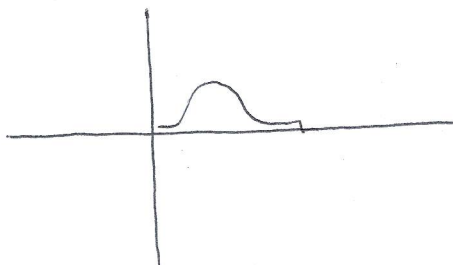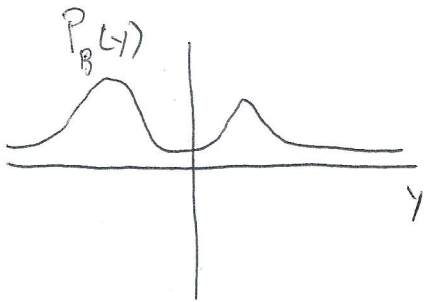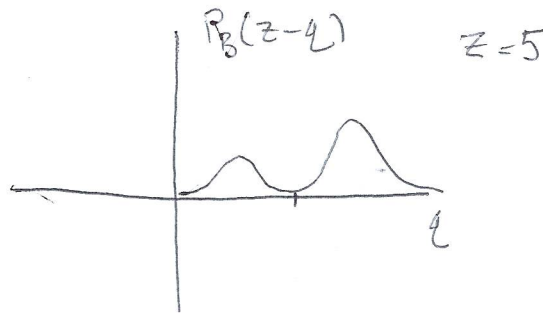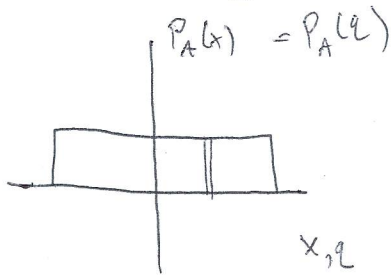
$$P_{A+B}(z) = \int_{-\infty}^{\infty} d\ell P_A(\ell) P_B(z-\ell) \quad \text{Convolution Integral}$$



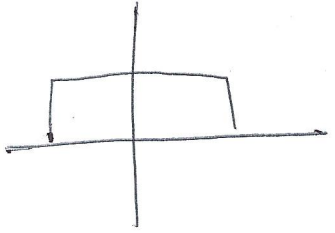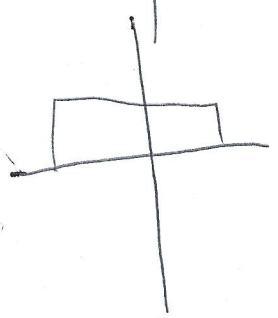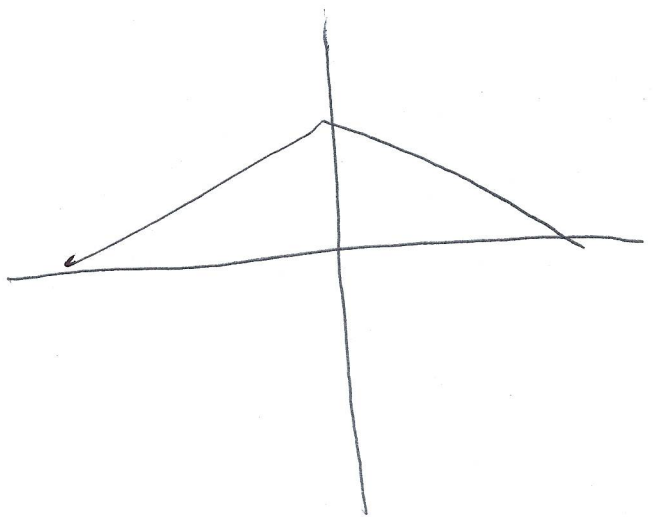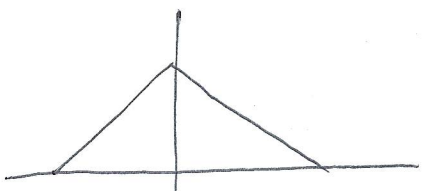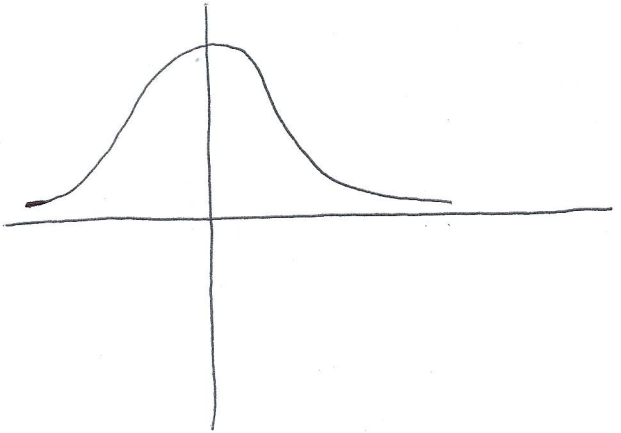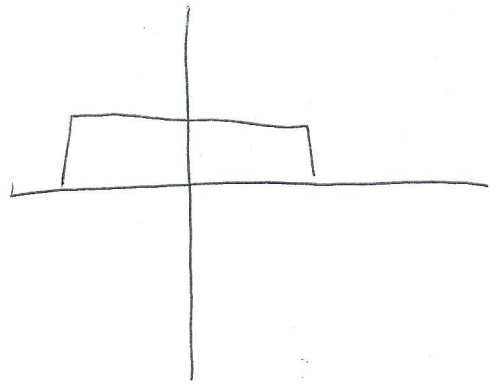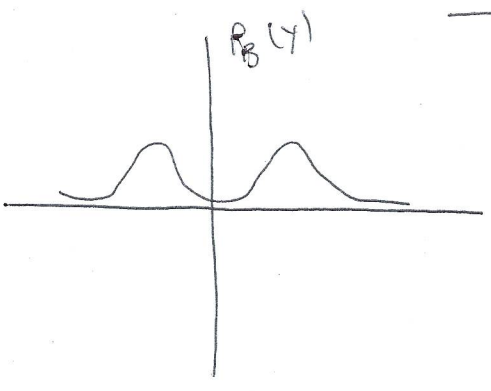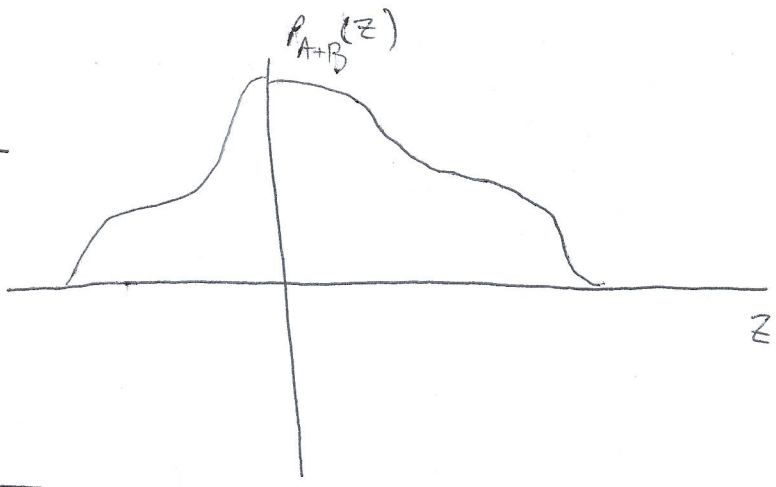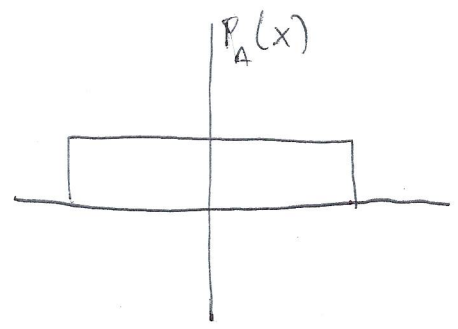

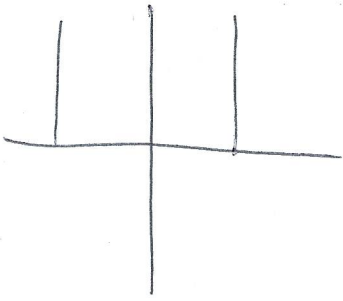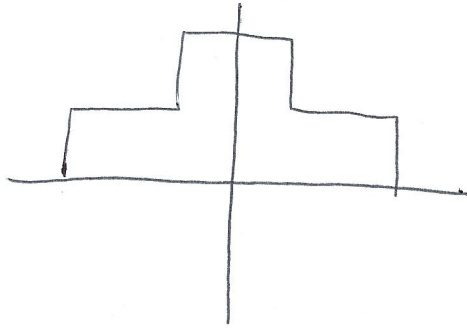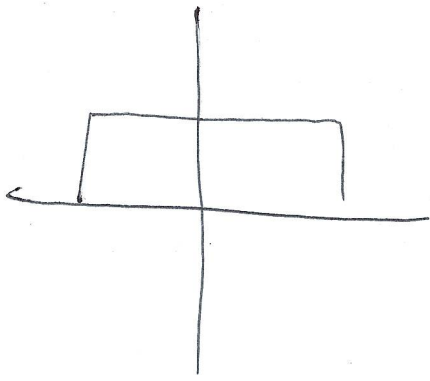

Central Limit Theorem

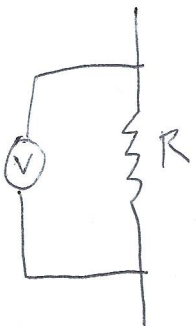

Thermal noise

Johnson noise

Nyquist noise


$$P = \frac{V^2}{R}$$

$$E = k_B T$$

$$P = E f = k_B T f$$


$$\frac{V^2}{R} = k_B T f \rightarrow V = \sqrt{4 R k_B T B}$$

B = bandwidth

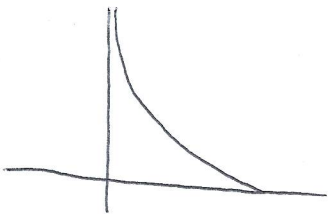


$$P(t) = \frac{1}{\tau} e^{-t/\tau}$$

Poisson Process

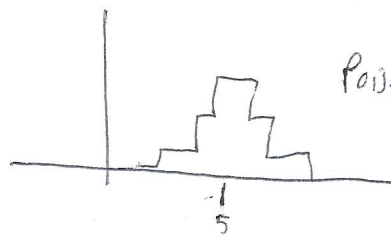


Poisson distribution

→ binomial distribution

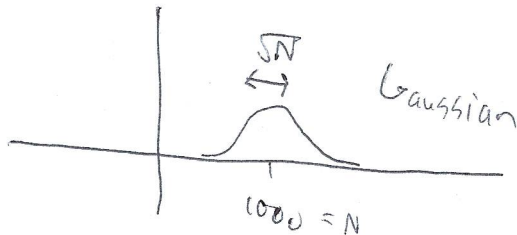

Gaussian

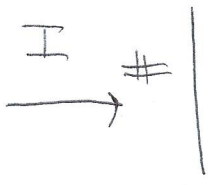

$\frac{1}{f}$  noise

$$\frac{1 \mu\text{A}}{1\text{C}} = \frac{10^{-12}}{10^{-19}} = 10^7$$